

CSCI 6461 Computer Systems Architecture

Single-Cycle Microarchitecture

Microarchitecture

2

- Microarchitecture is the specific hardware implementation of an instruction set architecture (ISA)
- It defines how instructions are executed through components like
 - datapaths,
 - control units, and
 - pipelines
- We will start with Single-Cycle Microarchitecture and move on to Pipeline Microarchitecture

Finite State Machine

3

- The architectural state for the ARM32 consists of 16 32-bit registers and the status register.
 - r0–r15, where r13 is sp, r14 is lr, and r15 is pc
- A microarchitecture must contain all of its **state**.
- Based on the current architectural state, the processor executes a particular instruction with a set of data to produce a new architectural state
- This is a type of Finite State Machine (**FSM**)

r0	00000000	NZCVI SVC
r1	00000000	
r2	00000000	
r3	00000000	
r4	00000000	
r5	00000000	
r6	00000000	
r7	00000000	
r8	00000000	
r9	00000000	
r10	00000000	
r11	00000000	
r12	00000000	
sp	00000000	
lr	00000000	
pc	00000000	
cpsr	000001d3	

Single-Cycle microarchitecture

4

- Single-cycle microarchitecture executes instructions in a **single cycle** .
 - fetch/decode/execute/write-back complete **within** the cycle
 - no pipeline => the clock period must be long enough to accommodate the slowest instruction
- Each instruction takes the same time (in reality they don't)
- State updates made at the end of an instruction's execution
- The slowest instruction determines cycle time
 - => long clock cycle times
 - this is a disadvantage

Instruction subset

5

To keep the microarchitectures easy to understand, we consider only a subset of the ARM instruction set:

- Memory instructions: `ldr`, `str` (with positive immediate offset)
- Data-processing instructions: `add`, `sub`, `and`, `orr`
- Branches: `b`
- We begin with `ldr`, `str` because, as the components used memory instructions can be reused in data processing instructions

6

The microarchitecture datapath

Datapath

7

- We divide our microarchitectures into two interacting parts:
 - the datapath and
 - the control unit
- The datapath operates on words of data
- It contains structures such as
 - memories
 - registers
 - ALUs, and
 - multiplexers.

Control Unit

8

- The control unit receives the current instruction from the datapath
 - and tells the datapath how to execute that instruction.
- The control unit produces
 - multiplexer select
 - register enable and
 - memory write signals
- This controls the operation of the datapath.

General Approach


9

- We begin with hardware containing the **state elements** .
- These elements include the memories and the architectural state
 - the program counter
 - registers, and
 - status register
- Then, we add blocks of combinational logic between the state elements to compute the new state based on the current state.

Single-cycle microarchitecture

10

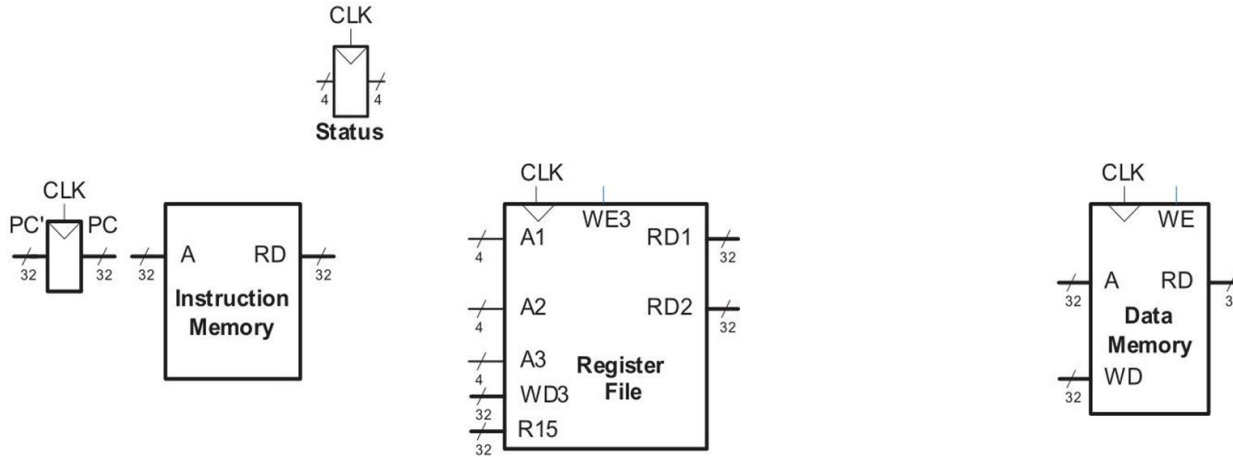- We begin constructing the datapath by connecting the state elements with combinational logic that can execute the various instructions.



A note on the pc

11

- Although the program counter (pc) is logically part of the register file
- it is read and written on every cycle independent of the normal register file operation
- it's more naturally built as a stand-alone 32-bit register.
- Its output, pc, points to the current instruction.
 - Its input, pc` indicates the address of the next instruction

Adding state elements

12

- Control signals determine which specific instruction is performed by the datapath at any given time.
- The control unit contains combinational logic that generates the appropriate control signals
 - based on the current instruction.
- We will gradually develop the single-cycle datapath, adding one piece at a time to the state elements.

Adding state elements


13

- The new connections are emphasized in black (or blue, for new control signals),
- whereas the hardware that has already been studied is shown in gray.
- The status register is part of the controller
 - and will be omitted while we focus on the datapath.

First Step

14

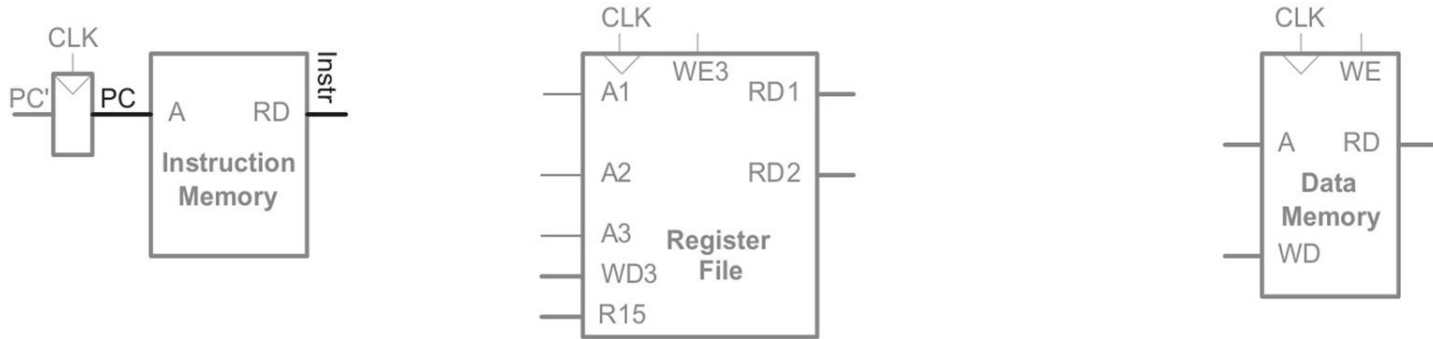- The program counter contains the address of the instruction to execute.
- The first step is to read this instruction from instruction memory.



PC connected

15

- The `pc` is connected to the address input of the instruction memory.
- The instruction memory reads out, or fetches, the 32-bit instruction, labeled **Instr**.
- The processor's actions depend on the specific instruction that was fetched.
- Lets look at `ldr/str` operations first


ldr Implementation

Example: `ldr r7, [r5, #8]`

Recap: Memory Instructions

17

Bit	\bar{I}	U
0	Immediate offset	Subtract offset from base
1	Register offset	Add offset to base

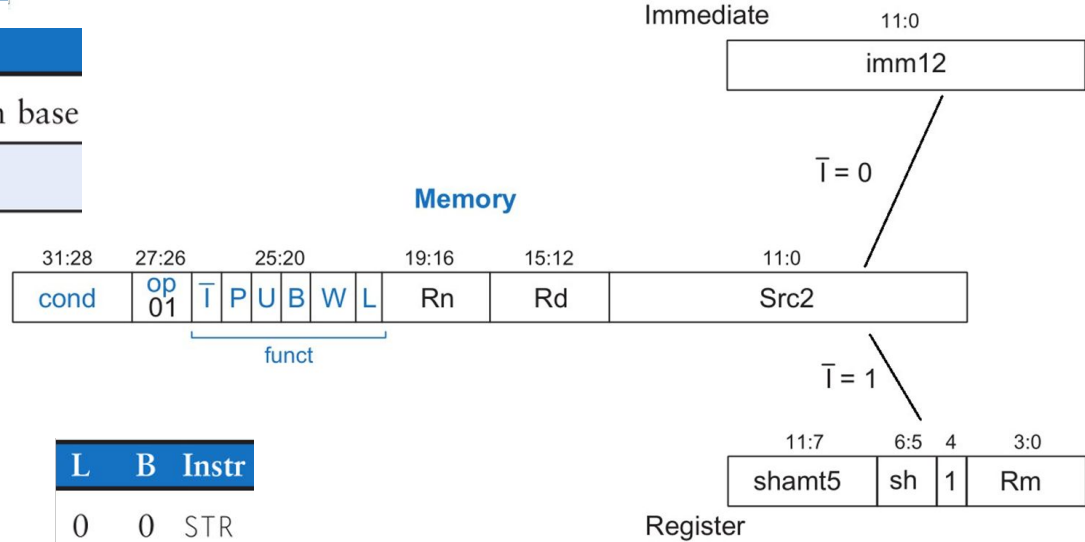

P	W	Index Mode
0	0	Post-index
0	1	Not supported
1	0	Offset
1	1	Pre-index


L	B	Instr
0	0	STR
0	1	STRB
1	0	LDR
1	1	LDRB

The offset is either a 12-bit unsigned immediate **imm12** or a register **Rm** that is optionally shifted by a constant **shamt5**.

ldr Example

18

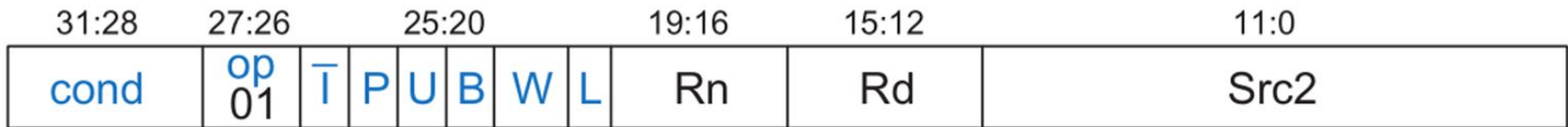- We start with `ldr` with **positive immediate offset** .
- For example, `ldr r7, [r5, #8]`
- For the `ldr` instruction, the next step is to read the source register containing the base address.
- This register is specified in the **Rn** field of the instruction.



The bits 19:16 of the instruction are connected to the address input of one of the register file ports, A1.

ldr r7, [r5, #8] Hex and Binary

19

Lets look at the hex and binary for

```
ldr r7, [r5, #8]
```

using CPUlator to generate the hex and then

<https://www.rapidtables.com/convert/number/hex-to-binary.html> to convert to binary:


Example `ldr r7, [r5, #8]`

20

- `ldr r7, [r5, #8]` = 0xe5957008
- 1110 = unconditional
- 01 = Memory Operation
 - 0 1 1 0 0 1
 - I P U B W L
 - Immediate (I bar), Offset (P/W), LDR (L/B), Add to base (U)
- 0101 = r5
- 0111 = r7
- 0000000001000 = #8

19:16(Rn) `ldr r7, [r5, #8]`


21

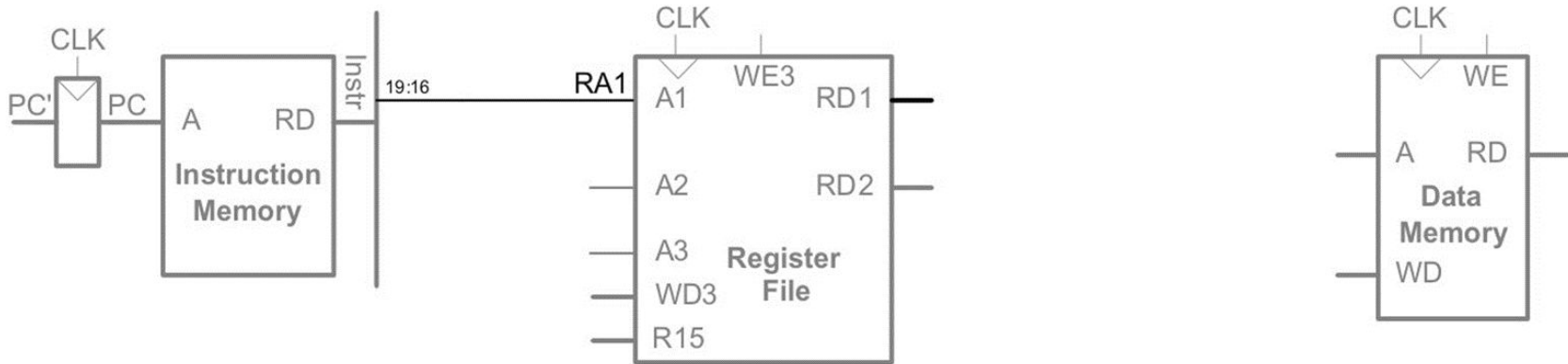

So the register address of the `ldr (r5)` is passed into the register file. The register file reads the register value onto RD1.

Zero extending `ldr r7, [r5, #8]`

22

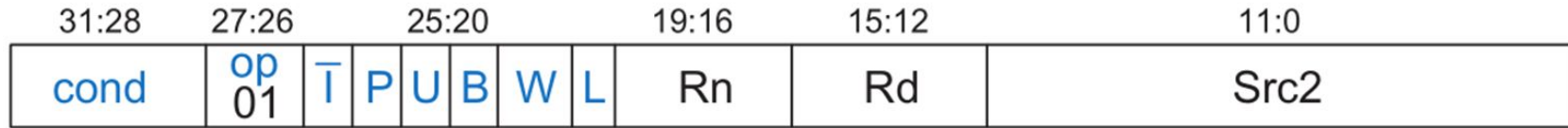


The offset, stored in the bits 11:0, is an unsigned value, so it must be zero-extended to 32 bits.

The 32-bit value is called
ExtImm

ImmExt31:12 = 0


ImmExt11:0 = Instr11:0

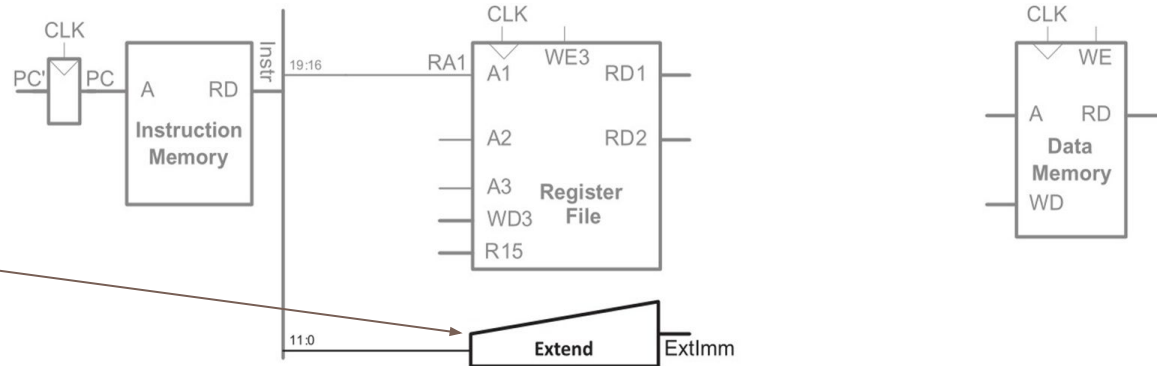

ALU Addition `ldr r7, [r5, #8]`

23

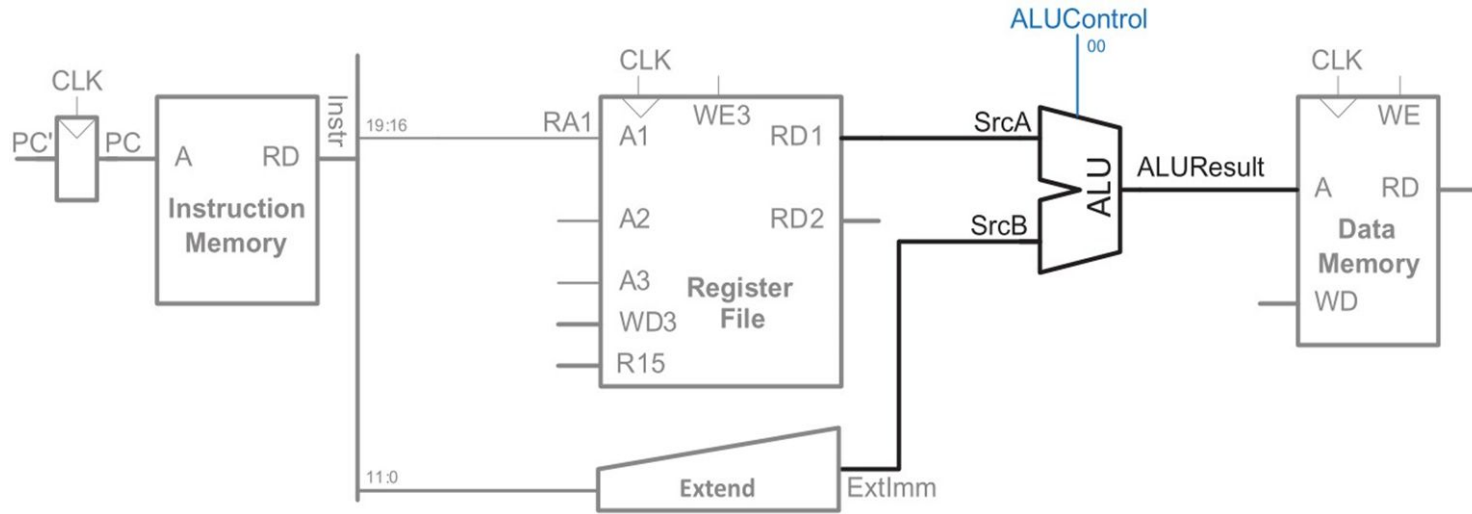The processor must add the base address to the offset to find the address to read from memory.



ALU Operations `ldr r7, [r5, #8]`

24


- For an LDR instruction, ALUControl should be set to 00 to perform addition
- ALUResult is sent to the data memory address to read.

<i>ALUControl</i>	Function
00	Add
01	Subtract
10	AND
11	OR


Read data memory `ldr r7, [r5, #8]`

25

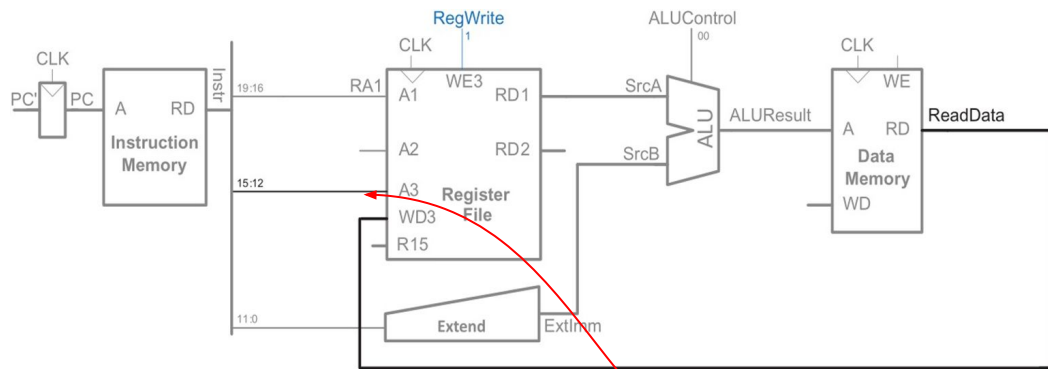The data is read from the data memory onto the ReadData bus and then written back to the destination register on the rising edge of the clock at the end of the cycle.



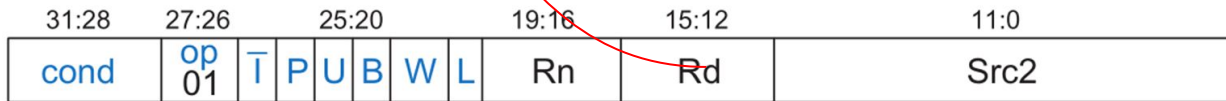
A control signal `RegWrite` is asserted so that the data value is written into the register file.



Next, increment PC'

26

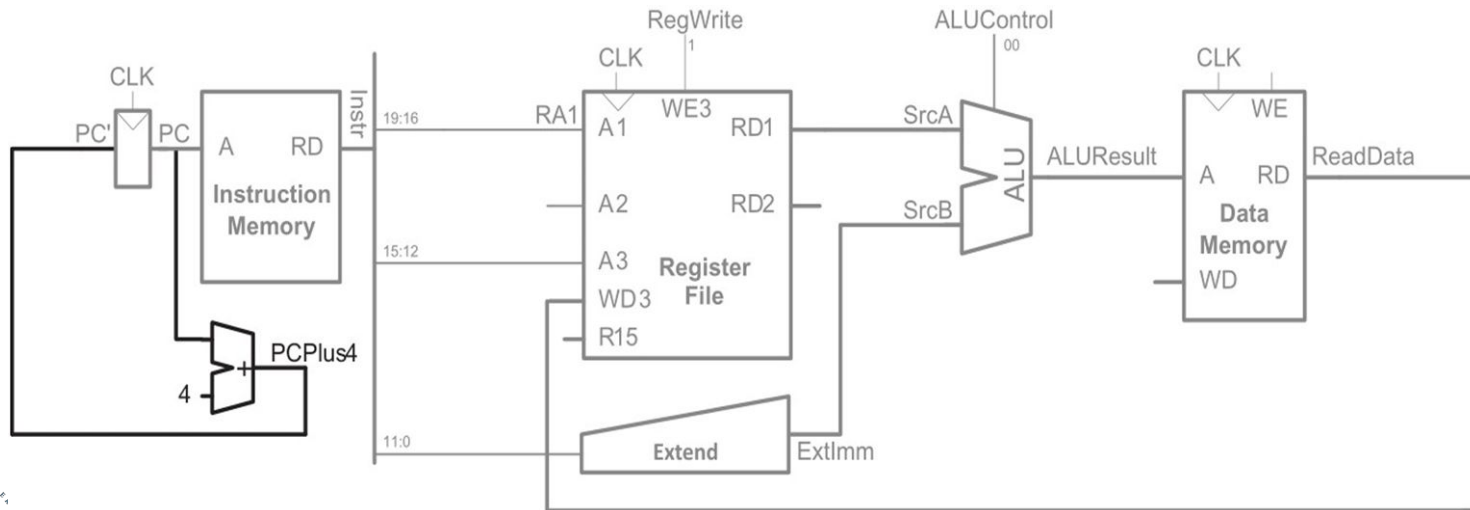While the instruction is being executed, the processor must compute the address of the next instruction, PC'



ldr ... finished

27

- The new address is written into the program counter on the next rising edge of the clock.
- This completes the datapath for the LDR instruction, except for the case of the base or destination register being R15.
- Note the increment applied to PC, +4 is added via the PCPlus4 block
 - While the instruction is being executed
- We will look at that case next


r15 Read

28

- In the ARM architecture, reading register R15 returns PC+8
- Another adder further increments the PC by 4.
- Writing register R15 updates the PC.
- PC' may come from the result of the instruction (ReadData) rather than PCPlus4.
- The PCSrc control signal is set to 0 to choose PCPlus4 or 1 to choose ReadData.
 - for example, `pop {pc}` requires a **ReadData**

Update the PC

29

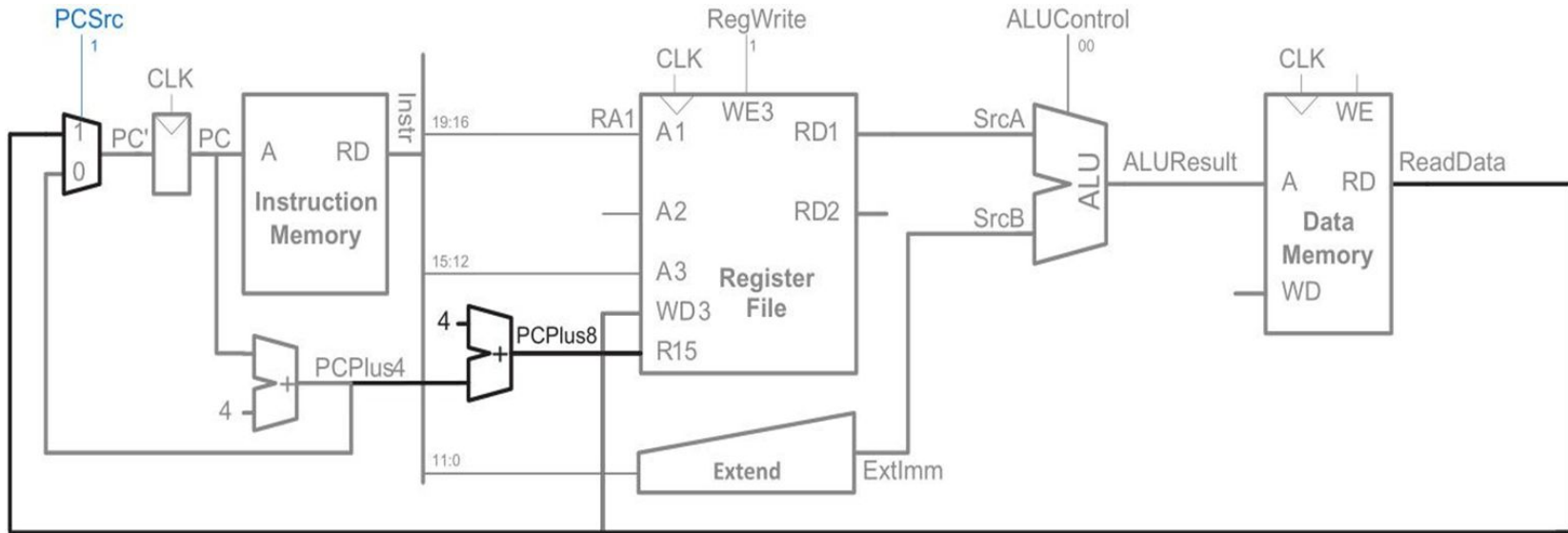

Extension to STR

Extend the previous example


str example

31

- Lets consider `str r7, [r5, #8]`
- Like `ldr`, `str` reads a base address from port 1 of the register file and zero-extends the immediate.
- The ALU adds the base address to the immediate to find the memory address.
- All of these functions are already supported in the datapath.
- The `str` instruction also reads a second register from the register file and writes it to the data memory.
- The Rd value is read onto the RD2 port **via RA2**.

Extension to `str r7, [r5, #8]`

32

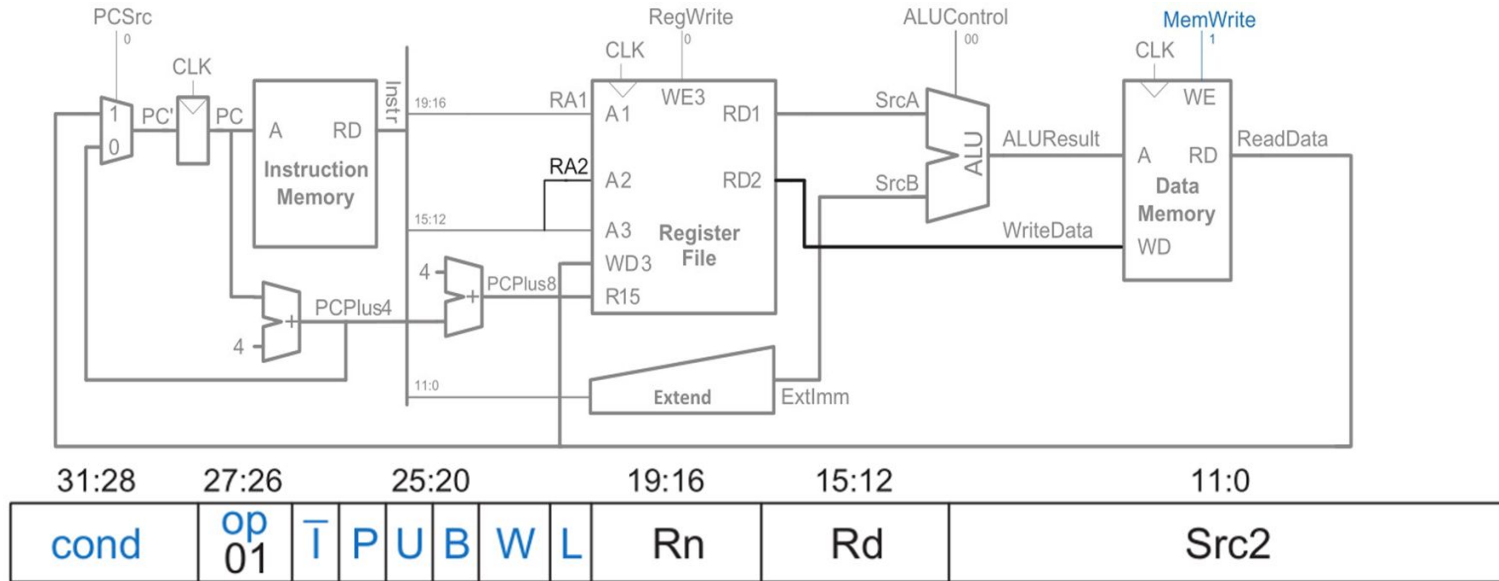

MemWrite=1 to write the data to memory; ALUControl=00 to add the base address and offset; RegWrite=0, because nothing should be written to the register file.

Finally

33

- Note that data is still read from the address given to the data memory
- Note again - RA2 is chosen from the Rd field (Instr15:12) for STR and the Rm field (Instr3:0) for data-processing instructions with register addressing based on the RegSrc control signal
- But that this ReadData is ignored
 - because RegWrite = 0.

Datapath enhancements

for add, sub, and, orr

add, sub, and, orr

35

- We now extend the datapath to handle the data-processing instructions,
 - add, sub, and, and orr,
 - using the immediate addressing mode.
 - Example: add r1, r2, #3
- add r1, r2, #3 reads a source register from the register file and an immediate from the low bits of the instruction
- performs ALU Add operation on them,
 - and writes the result back to register Rd (R1)


add, sub, and, orr

36

- These instructions are similar
- Hence, they can all be handled with the same hardware
- But using different **ALUControl** signals.
- The ALU also produces four flags, ALUFlags 3:0 (Negative, Zero, Carry, oVerflow),
 - that are sent back to the controller.

Example add r1, r2, #3

37

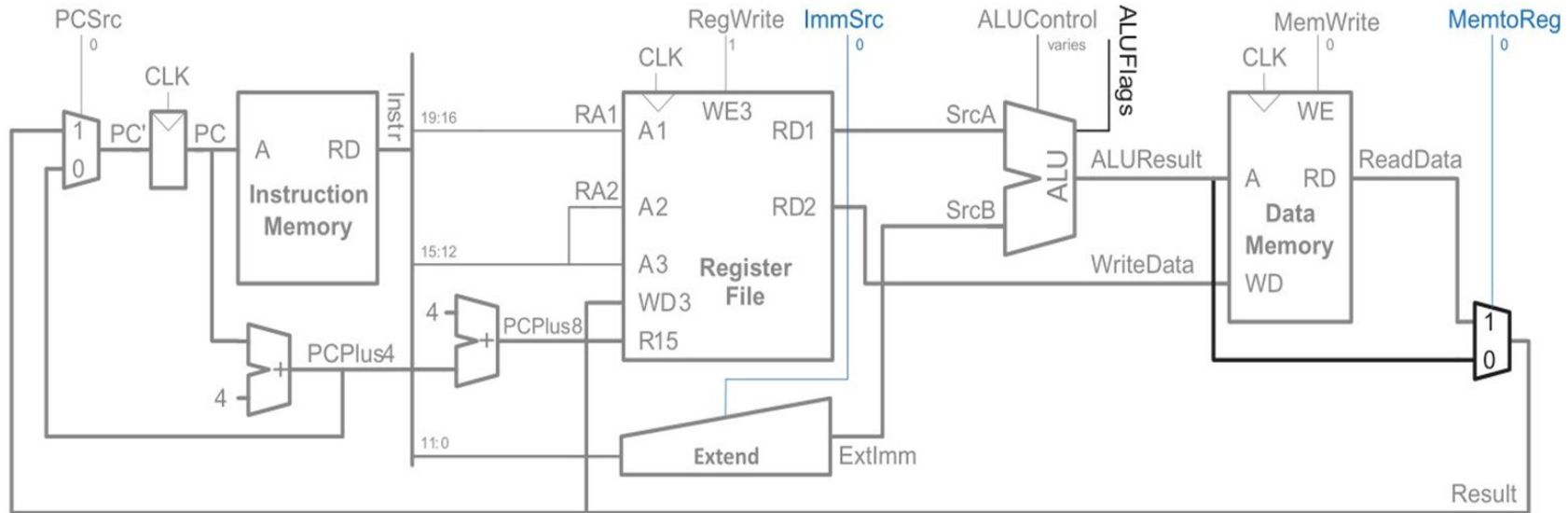

31:28	27:26	25:20	19:16	15:12	11:0
cond	op	funct	Rn	Rd	Src2
4 bits	2 bits	6 bits	4 bits	4 bits	12 bits

ImmSrc role

38

- Data-processing instructions use only an 8-bit immediate rather than a 12-bit immediate.
- Therefore, we provide the ImmSrc control signal to the Extend block.
- When it is 0,
 - ExtImm is zero-extended from Instr7:0 for data-processing instructions.
- When it is 1,
 - ExtImm is zero-extended from Instr11:0 for `ldr` or `str`.

Additional Multiplexer


39

- For `ldr`, the register file received its write data from the data memory.
- However, data-processing instructions write `ALUResult` to the register file.
- Therefore, we add another multiplexer to choose between `ReadData` and `ALUResult`.
- We call its output **Result**.

MemtoReg Multiplexer


40

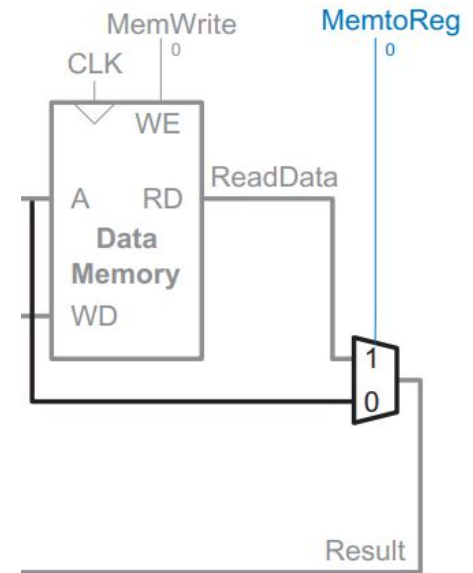- The multiplexer is controlled by another new signal, MemtoReg.
- MemtoReg is 0 for data processing instructions to choose Result from ALUResult;
- it is 1 for `ldr` to choose ReadData.



Finally

41

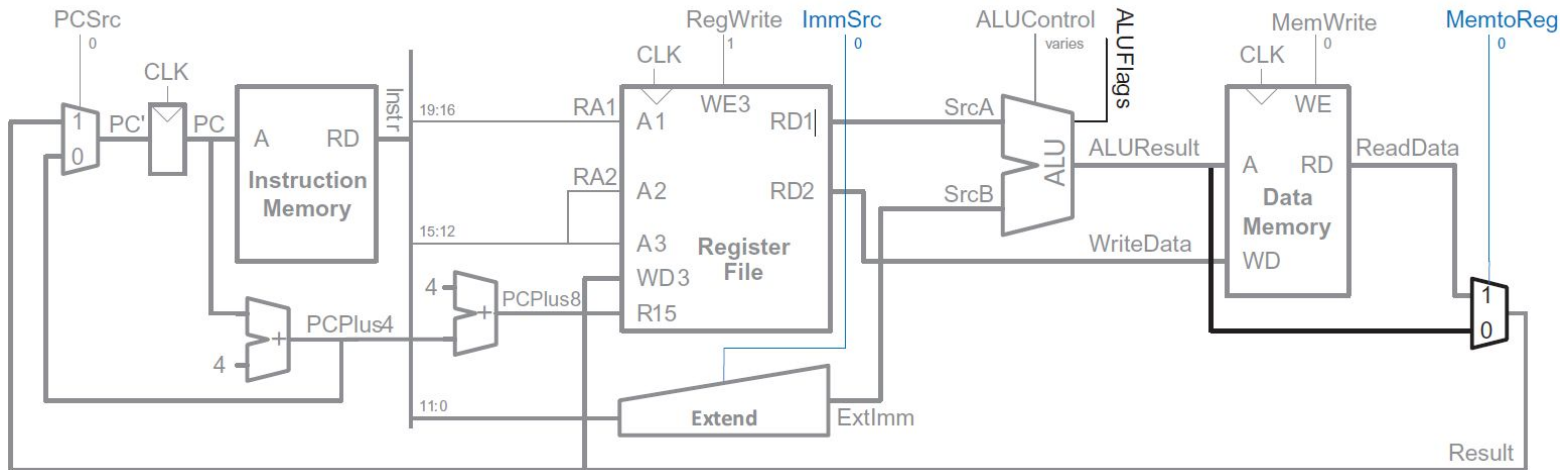

The microarchitecture for add r1, r2, #3

31:28	27:26	25:20	19:16	15:12	11:0
cond	op	funct	Rn	Rd	Src2
4 bits	2 bits	6 bits	4 bits	4 bits	12 bits


DP and Register Addressing

```
add r1, r2, r3
```

Example: add r1, r2, r3

43

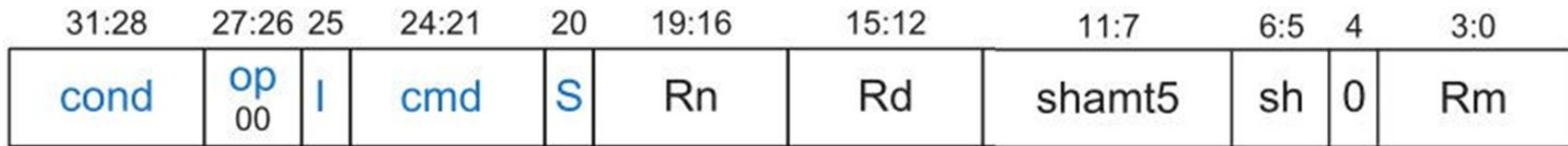
- Example: add r1, r2, r3
- Data-processing instructions with register addressing receive their 2nd source from **Rm**, specified by Instr3:0




We must add multiplexers on the inputs of the register file and ALU to select this second source register.

Multiplexers - RegSrc and ALUSrc

44

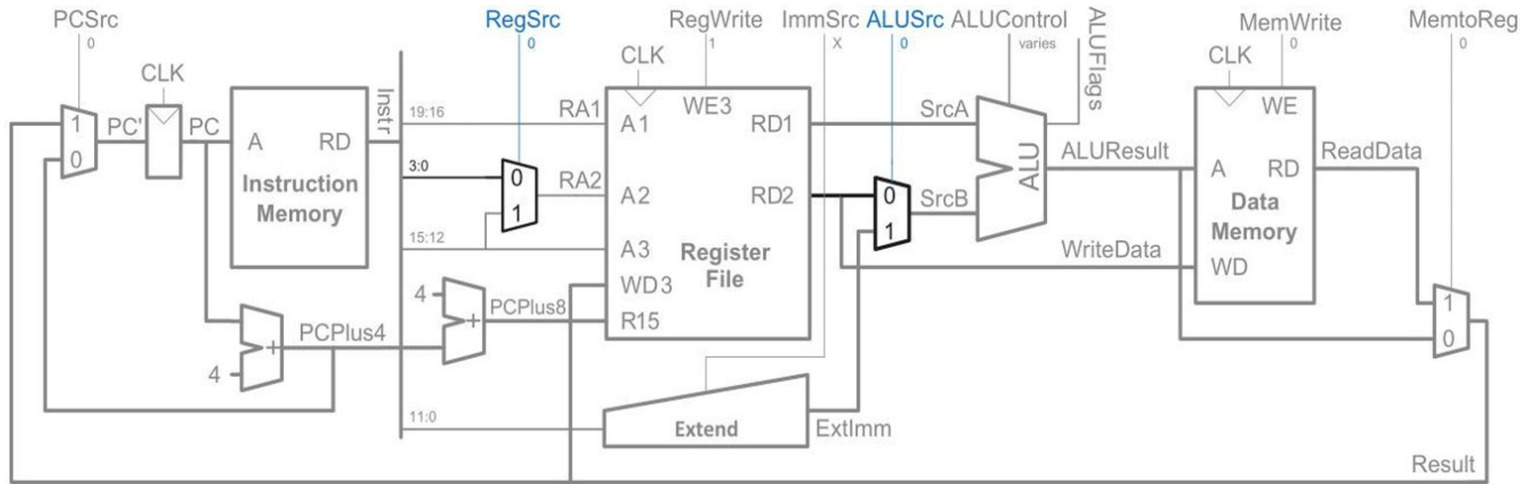

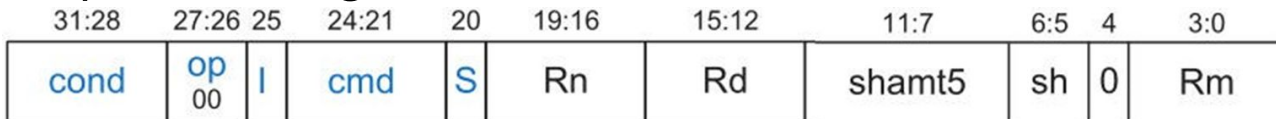RegSrc - Select from Instr15:12 for STR and the **Rm** field (Instr3:0) for data-processing. **ALUSrc** select between ExtImm or RD2



RegSrc and ALUSrc

45

- RA2 is chosen from
 - Rd field (Instr15:12) for STR and
 - Rm field (Instr3:0) for data-processing instructions with register addressing
- based on the **RegSrc** control signal
- Based on the **ALUSrc** control signal, the second source to the ALU is selected from ExtImm for instructions using immediates
 - and from the register file for data-processing instructions with register addressing.

Data processing & Branching

The b instruction

Immsrc and the b instruction

47

- The branch instruction adds a 24-bit immediate to PC+8
 - and writes the result back to the PC.
- The immediate is multiplied by 4 and sign extended.
- Therefore, the Extend logic needs yet another mode.

ImmSrc is increased to 2 bits

ImmSrc	ExtImm	Description
00	{24 0s} <i>Instr</i> _{7:0}	8-bit unsigned immediate for data-processing
01	{20 0s} <i>Instr</i> _{11:0}	12-bit unsigned immediate for LDR/STR
10	{6 <i>Instr</i> ₂₃ } <i>Instr</i> _{23:0} 00	24-bit signed immediate multiplied by 4 for B

Signed immediate extension


48

The code $\{6 \text{ Instr}_{23}\} \text{ Instr}_{23:0} 00$ is understood in two steps

- The shift left by 2 means the 2 LSB are zero filled
- And the remaining space (6 bits) get their value from the Instr_{23} field - which of course is sign extended
- This effectively gives an addressable range of
 - Range = $\pm (2^{25})$ bytes = ± 32 MB
 - Because we need one bit for the sign (hence the 2^{25})

Datapath with Branching

49

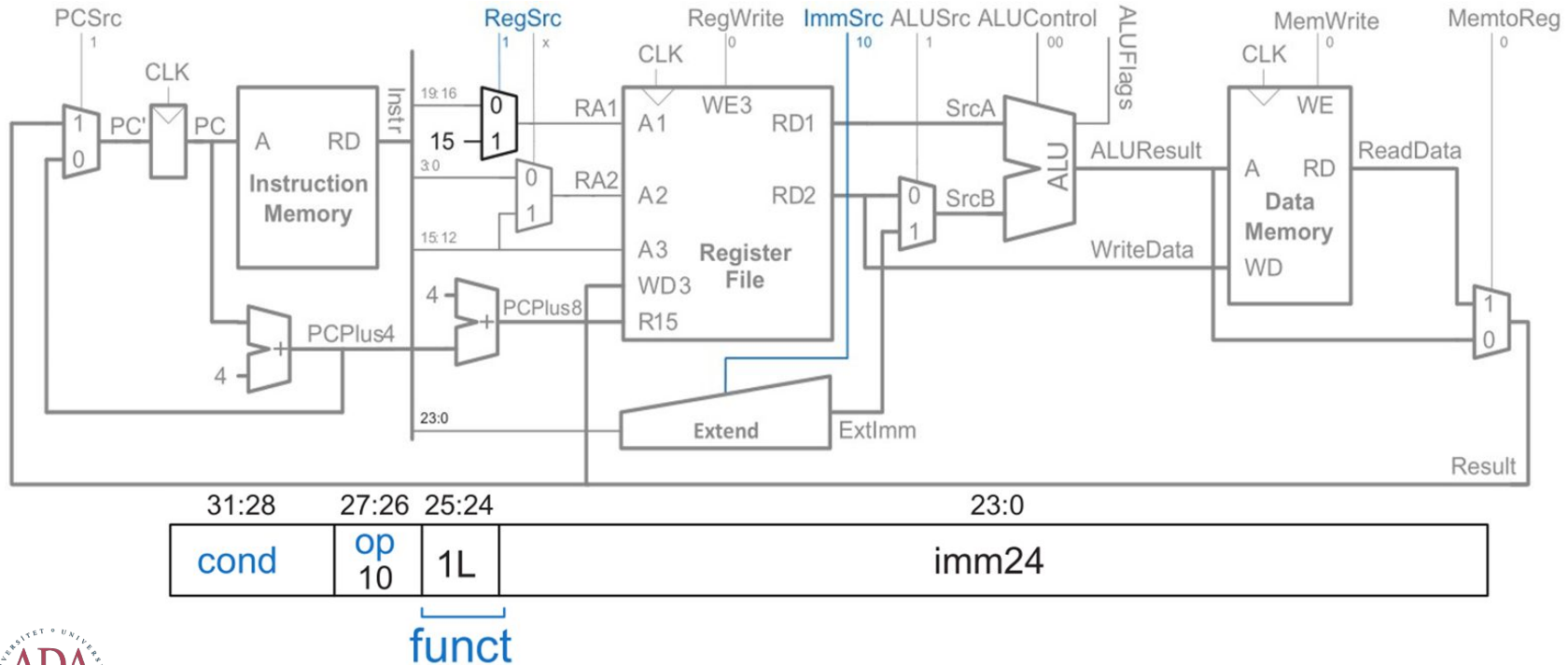

Note that RegSrc now becomes a two-bit control signal and is connected to two multiplexers as discussed next

Datapath with Branching

50

- PC+8 is read from the first port of the register file.
- Therefore, a multiplexer is needed to choose R15 as the RA1 input.
- It is controlled by another bit of **RegSrc**, choosing $\text{Instr}_{19:16}$ for most instructions but 15 for b
- MemtoReg is set to 0 and PCSrc is set to 1 to select the new PC from ALUResult for the branch
- This is pc-relative addressing as mentioned


51

Control Unit

Control Unit


52

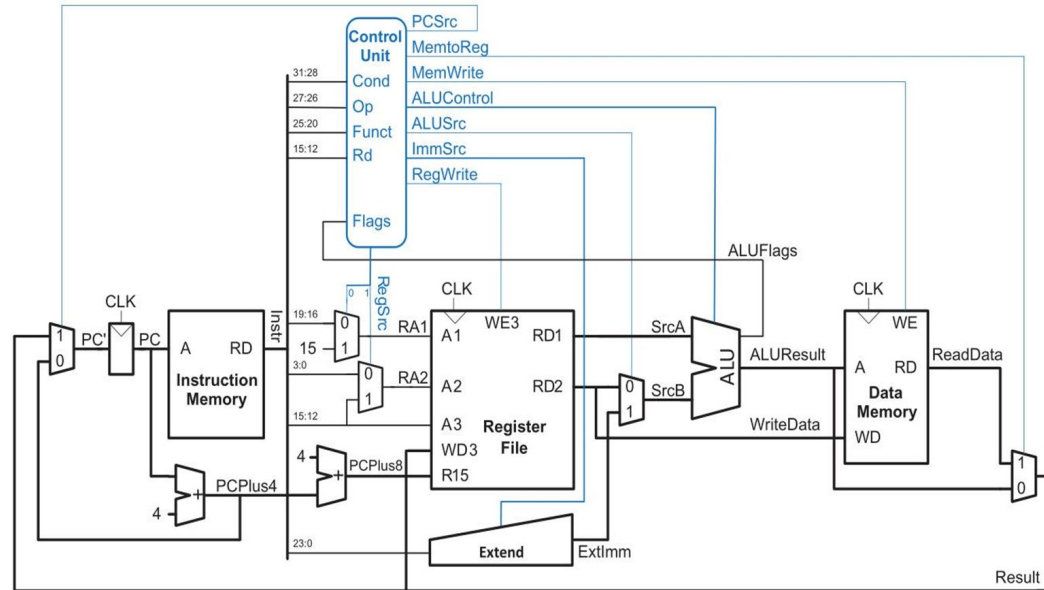The control unit computes the control signals based on the **cond**, **op**, **funct** fields of the instruction ($\text{Instr}_{31:28}$, $\text{Instr}_{27:26}$, $\text{Instr}_{25:20}$) as well as the flags and whether the destination register is the PC.



Control Unit

53

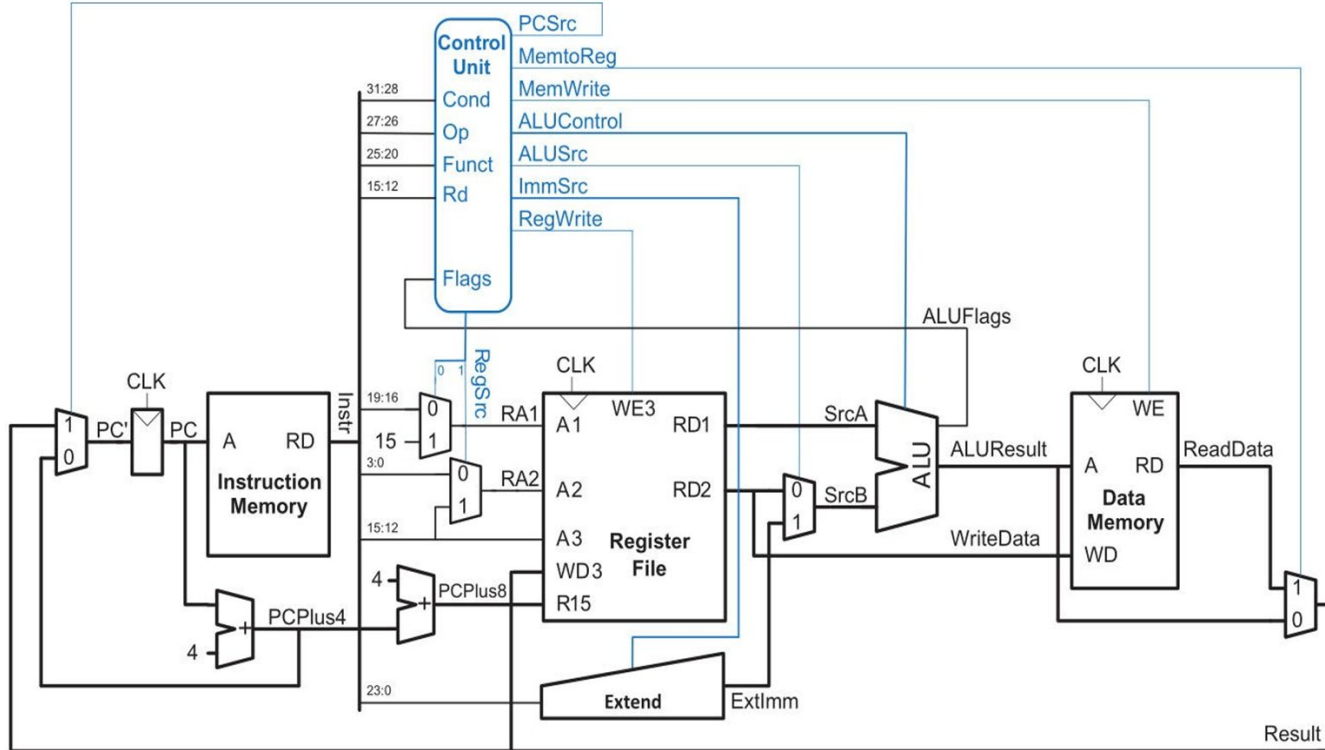


Conditional Logic

54

The conditional logic maintains the status flags and only enables updates to architectural state when the instruction should be conditionally executed.

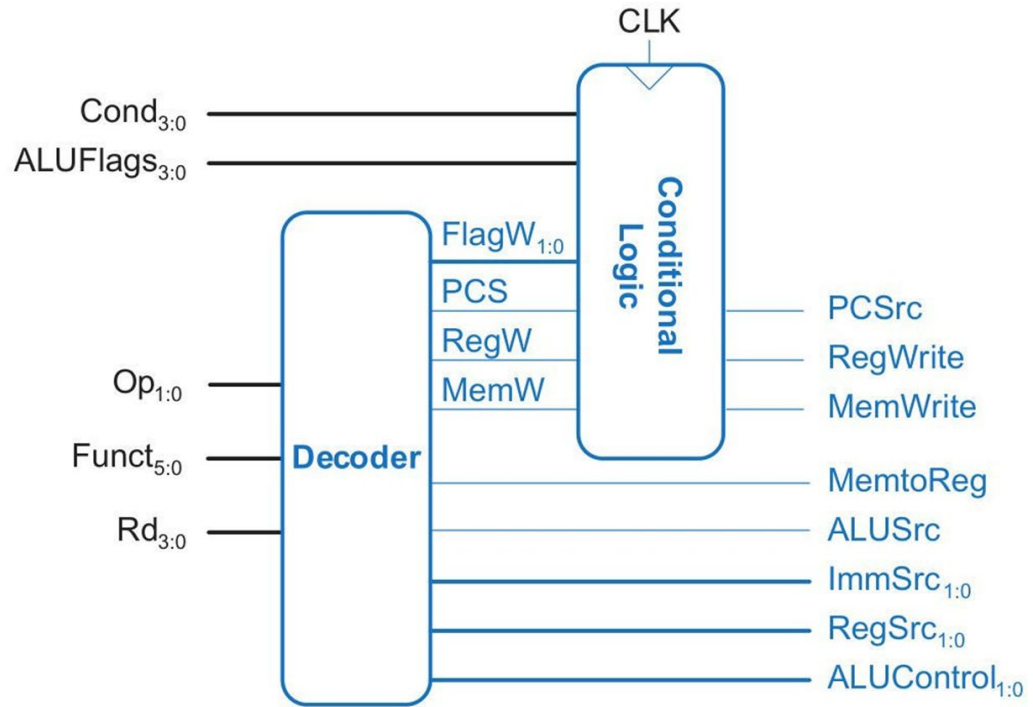The decoder generates control signals based on Instr.




Main decoders

55

- The main decoder produces most of the control signals.
- The ALU decoder uses the **funct** field to determine the type of data-processing instruction.
- The PC Logic determines whether the PC needs updating due to a branch or a write to R15.

Decoder and Conditional Logic

56

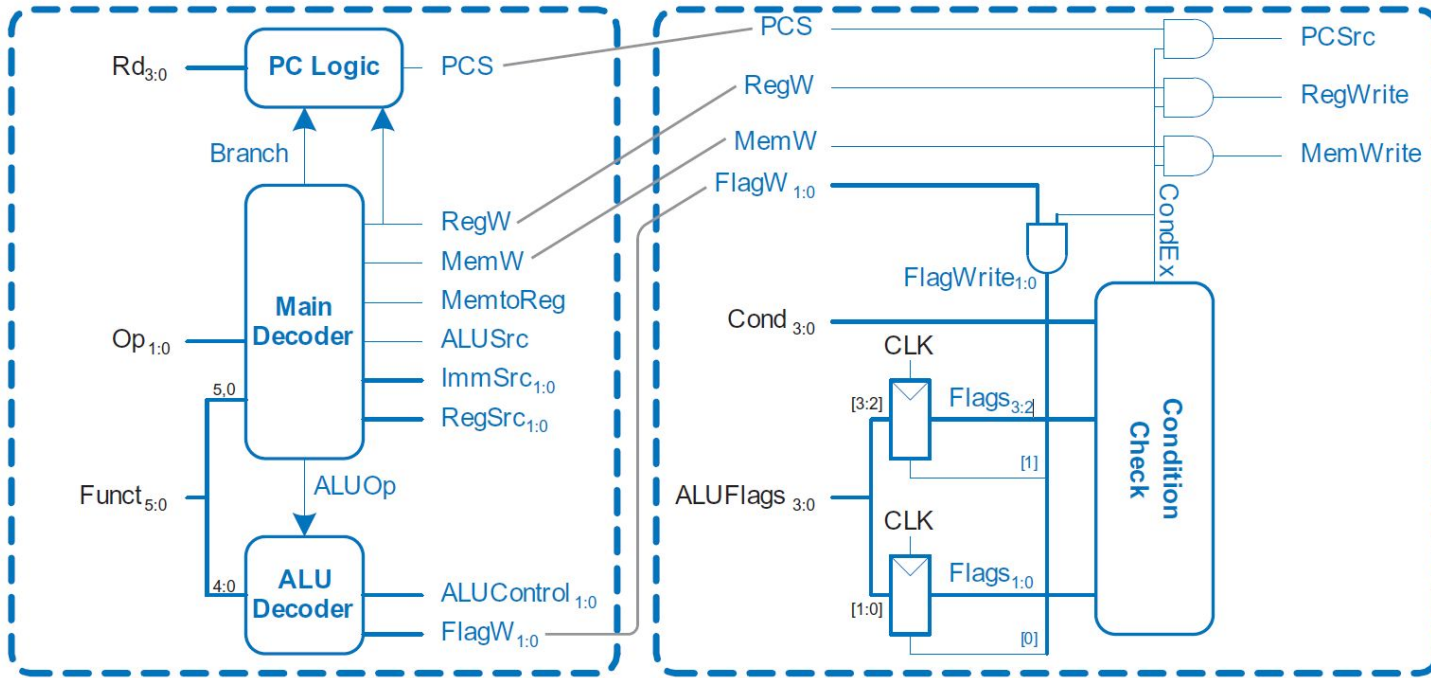

Decoder and Conditional Logic

57

The controller is in two main parts:

- the **Decoder** which generates control signals based on Instr, and the
- **Conditional Logic** which maintains the status flags and only enables updates to architectural state when the instruction should be conditionally executed
- The **Conditional Logic** , determines whether the instruction should be executed (CondEx) based on the cond field and the current values of the N, Z, C, and V

- ALUSrc control signal:
 - the second source to the ALU is selected from ExtImm for instructions using immediates (ALUSrc=1)
 - and from the register file for data-processing instructions with register addressing (ALUSrc=0)

Register Source: **RegSrc**

59

In the following examples we consider only these operations:


- DP with Regs
- DP with Immediates
- LDR with Immediates
- STR with Immediates
- Branching

For the sake of simplicity, LDR/STR with registers is omitted, which in turn simplifies the **RegSrc** control path

RegSrc bit ordering (simplified)

60

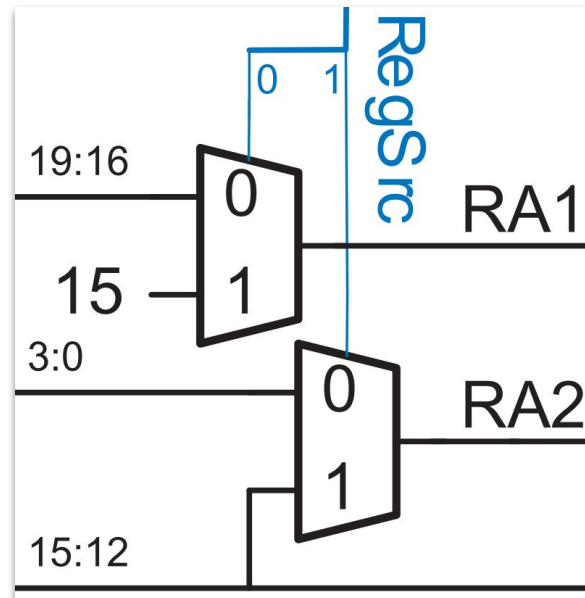- 00: RA1 gets 19:16, RA2 gets 3:0
 - DP with Regs
- 0X: RA1 gets 19:16, RA2 don't care
 - DP with Imm
 - LDR with Imm
- 01: RA1 gets 19:16, RA2 gets 15:12
 - STR with Imm (2 reads)
- 1X: RA1 gets R15, RA2 don't care
 - Branch



Main decoder truth table

61

Op	Funct ₅	Funct ₀	Type	Branch	MemtoReg	MemW	ALUSrc	ImmSrc	RegW	RegSrc	ALUOp
00	0	X	DP Reg	0	0	0	0	XX	1	00	1
00	1	X	DP Imm	0	0	0	1	00	1	0X	1
01	X	0	STR	0	X	1	1	01	0	01	0
01	X	1	LDR	0	1	0	1	01	1	0X	0
10	X	X	B	1	0	0	1	10	0	1X	0

Where op: 00 = DP, 01 = Memory, 10 = B

The main decoder determines the type of instruction: data-processing register, data-processing immediate, STR, LDR, B. It sends **MemtoReg**, **ALUSrc**, **ImmSrc1:0**, and **RegSrc1:0** directly to the datapath.

DP Example (op=00): `add r0, r1, r2`

62

Op	Funct ₅	Funct ₀	Type	Branch	MemtoReg	MemW	ALUSrc	ImmSrc	RegW	RegSrc	ALUOp
00	0	X	DP Reg	0	0	0	0	XX	1	00	1

funct₅ (I) = 0: Register Value, not immediate

funct₀ (S) = X: don't care

Branch = 0: no branch

MemtoReg = 0: this is RegW

ALUSrc = 0: Use RD2

ImmSrc = XX: don't care

RegSrc = 00: 19:16 and 3:0

25	24:21	20
I	cmd	S

ImmSrc	ExtImm	Description
00	{24 0s} Instr _{7:0}	8-bit unsigned immediate for data-processing
01	{20 0s} Instr _{11:0}	12-bit unsigned immediate for LDR/STR
10	{6 Instr ₂₃ } Instr _{23:0} 00	24-bit signed immediate multiplied by 4 for B

31:28	27:26	25	24:21	20	19:16	15:12	11:7	6:5	4	3:0
cond	op	I	cmd	S	Rn	Rd	shamt5	sh	0	Rm
	00									

(op=01) str with positive immediate

63

Op	Funct ₅	Funct ₀	Type	Branch	MemtoReg	MemW	ALUSrc	ImmSrc	RegW	RegSrc	ALUOp
01	X	0	STR	0	X	1	1	01	0	10	0
31:28		27:26		25:20		19:16		15:12		11:0	
cond		op 01	\bar{T}	P	U	B	W	L	Rn	Rd	Src2

func₅ (lbar) = X: don't care

func₀ (L) = 0: not a LDR

Branch = 0: no branch

MemtoReg = X: don't care

ALUSrc = 1: Imm, no 2nd reg

ImmSrc = 01: 12-bit zero extended

RegSrc = 01: 19:16 (RA1) and 15:12 (RA2)

ALU Decoder Truth Table

64

The ALUControl asserts FlagW to update the status flags when the S-bit is set.

add, sub update all flags (11), whereas and, orr only update the N and Z flags. (10)

<i>ALUOp</i>	<i>Funct_{4:1}</i> (cmd)	<i>Funct₀</i> (S)	Type	<i>ALUControl_{1:0}</i>	<i>FlagW_{1:0}</i>
0	X	X	Not DP	00 (Add)	00
1	0100	0	ADD	00 (Add)	00
		1			11
	0010	0	SUB	01 (Sub)	00
		1			11
	0000	0	AND	10 (And)	00
		1			10
	1100	0	ORR	11 (Or)	00
		1			10

PC Logic

65

The PC Logic checks if the instruction is a write to `r15` or a branch such that the PC should be updated

$$PCS = ((Rd == 15) \&\& RegW) \mid\mid Branch$$

PCS may be killed by the conditional logic before it is sent to the datapath as PCSrc.

Conditional Logic

66

- The conditional logic determines whether the instruction should be executed (CondEx) based on the cond field and the current values of the N, Z, C, and V flags (Flags3:0).
- If the instruction should not be executed, the write enables and PCSrc are forced to 0 so that the instruction does not change the architectural state.
- The conditional logic also updates some or all of the flags from the ALUFlags when FlagW is asserted by the ALU Decoder and the instruction's condition is satisfied (CondEx = 1).

Summary

67

We have discussed the following topics

- Single Cycle Microarchitecture
- Datapaths for Memory, Data Processing and Branching examples
- Control unit
 - Multiplexers
 - Truth Tables and decoder Logic
 - Conditional Logic

